

Fire Detector and alarm indication using 8051

Fire detection and alarm system is very important to avoid major accidents which are caused due to fire. Fire may cause a big loss or damage to any property, home, company, warehouse, mall, or bazaar. It also causes severe injuries to human lives. And that is the reason fire detection systems are very important in the day today's life. In the mini project category, we have added a fire detection alarm system using an 8051 microcontroller.

Description of the project:

On our website, we have a [list of sensor based projects](#). This is a mini project, in this project basically, we have used a smoke sensor to detect smoke and fire.

In this project, we have used an 89s51 microcontroller and a smoke sensor. For smoke detection, we have used an MQ9 gas sensor which detects carbon monoxide and even LPG, and methane. This sensor is very useful for the detection of gas leakage. If smoke is detected then this sensor gives high output to the comparator. Then comparator gives high pulse output to the microcontroller. Due to the fast response of the sensor, we can take immediate action on it and can stop further damage. With the help of smoke sensors, we can detect fire or smoke.

This project is very useful to warn people about the fire. Fire can cause the death of many. It is also hazardous to the workstation, and home. With this low-cost fire detector mini-project, we can warn people. Fire accidents can occur at any place but it is quite difficult for everyone to install a fire alarm system in their home or shop. In such situations, our low-cost fire detector is very useful. The main advantage of this project is its cost-effectiveness.

Description in detail:


Gas sensor output is in analog format. This analog voltage can not be given to the 8051 microcontroller since it requires digital input. So we have to either interface analog to digital convertor or comparator between sensor and microcontroller. To reduce the cost and reduce the circuit size, we have chosen to add a comparator to this circuit.

We have also provided a buzzer for alarm indication. If smoke is detected then the buzzer will be turned on. We have also used a 16 by 2 LCD display in this project. It displays the name of the project as well as it displays different messages.

This is one of the important low cost microcontroller based projects. We have used an MQ9 sensor for smoke detection. If the sensor crosses the threshold value then the buzzer will be turned on. LCD displays a message as smoke detected.

This project is very useful in homes, warehouses, banks, malls, and stations to alert people. This helps to avoid major accidents due to fire and smoke.

Block Diagram of the project:

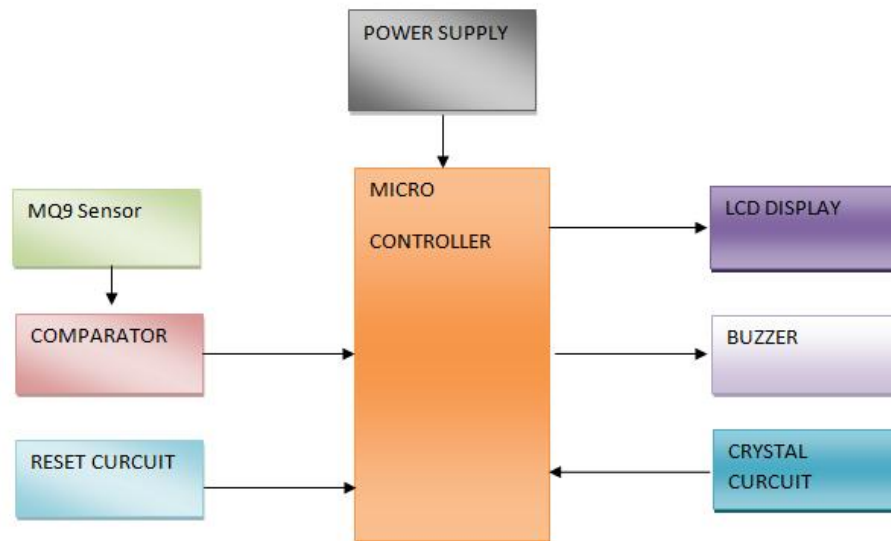

Hardware Specifications

This fire detection and alarm system uses several critical components. Each part plays a specific role in ensuring the system functions effectively. Here's a detailed explanation of the components used:

1. Microcontroller (89S51 – 8051 Series Microcontroller)

The **89S51 microcontroller** is the core of the system. It processes signals from the sensor and controls the outputs such as the buzzer and LCD. The 89S51 belongs to the **8051 microcontroller family** and includes:

- **4KB of Flash Memory:** Stores the program code.
- **128 bytes of RAM:** Handles temporary data storage during operations.
- **I/O Ports:** Interfaces with other components like the comparator, buzzer, and LCD.
- **Timers:** Ensures precise timing for various operations.

2. MQ9 Sensor (Smoke Sensor)

The **MQ9 sensor** detects harmful gases such as carbon monoxide, methane, and LPG. It is used here to identify smoke or fire.

- The sensor outputs an **analog signal** proportional to the gas concentration.
- The system uses this signal to determine whether the smoke level exceeds the predefined threshold.
- The sensor is fast, sensitive, and cost-effective, making it ideal for real-time fire detection.

3. Comparator

A **comparator** is used to convert the analog signal from the MQ9 sensor into a digital signal that the microcontroller can process.

- It compares the sensor's output voltage with a reference voltage.
- If the sensor output exceeds the reference value, the comparator generates a **high pulse** to alert the microcontroller.
- This simplifies the circuit design and reduces cost compared to using an analog-to-digital converter (ADC).

4. LCD Display (16x2)

The **16x2 LCD** is used to provide visual feedback and messages to the user.

- It displays system status, such as "Smoke Detected" or the name of the project.
- It has two rows and 16 columns, allowing clear and concise messaging.
- The LCD communicates with the microcontroller through its I/O pins.

5. Transistor, Crystal, Diodes, Resistors, and Capacitors

These passive and active components are crucial for the stability and functionality of the circuit:

- **Transistor:** Acts as a switch or amplifier to control the buzzer or other peripherals.
- **Crystal Oscillator:** Provides the clock signal for the microcontroller, ensuring accurate timing.
- **Diodes:** Used for rectification and to protect the circuit from reverse voltage.
- **Resistors:** Control current flow and set reference voltages for the comparator.

- **Capacitors:** Used for filtering and stabilizing the power supply.

6. Buzzer

The **buzzer** provides an audible alarm to alert people when smoke or fire is detected.

- It is activated by the microcontroller when the threshold is crossed.
- The loud sound ensures immediate attention in case of emergencies.


7. Transformer, Voltage Regulator, and Power Supply

The **power supply** ensures all components receive the required voltage for operation.

- **Transformer:** Steps down the high AC voltage from the mains to a lower AC voltage suitable for the circuit.
- **Voltage Regulator:** Converts the stepped-down AC voltage to a steady **5V DC** required by the microcontroller and other components.
- **Power Supply Unit:** Provides clean and stable DC power to ensure reliable system performance.

These components collectively make the fire detection and alarm system reliable, efficient, and cost-effective, ensuring real-time detection and quick response in case of fire or smoke.

Circuit Diagram :

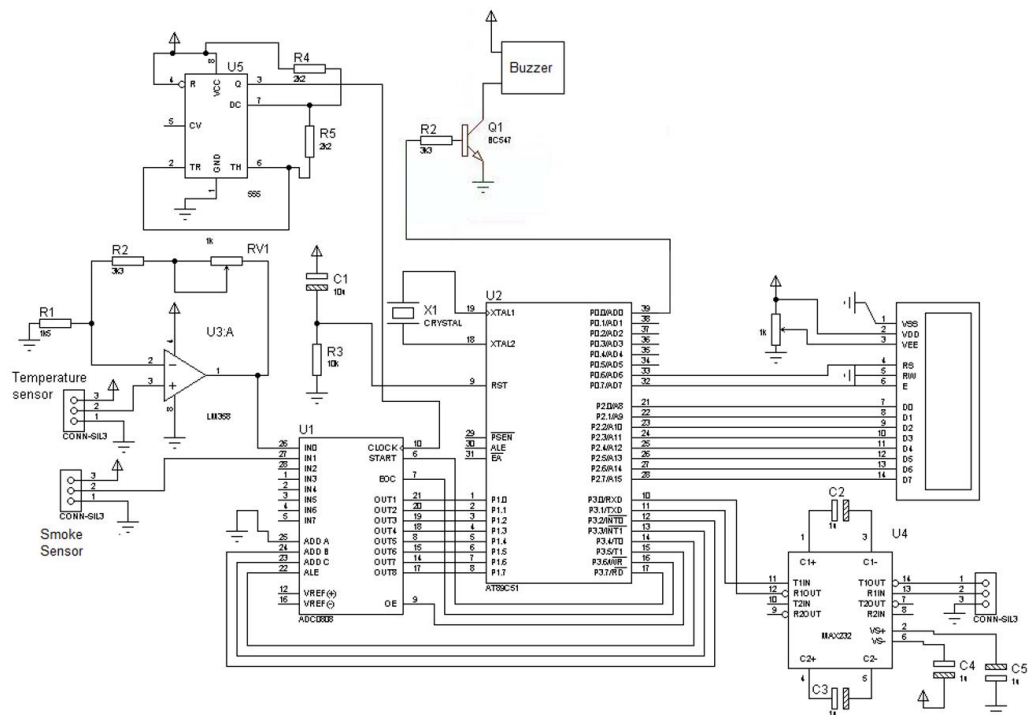

Project Photographs



Conclusion

The **Fire Detection and Alarm System using the 8051 Microcontroller** is an efficient, cost-effective solution for fire safety. By integrating a sensitive MQ9 smoke sensor, a responsive alarm mechanism, and a clear LCD display, this system provides real-time alerts that can help prevent fire-related accidents and reduce damage. Its simple design, affordability, and ease of use make it suitable for various applications, including homes, warehouses, malls, and workplaces.

The project demonstrates how low-cost hardware components can be combined to create a reliable safety system. The use of a comparator for analog-to-digital conversion simplifies the circuit and reduces costs without compromising performance. Additionally, the fast response of the MQ9 sensor ensures quick detection of smoke or gas leaks, enabling timely actions to prevent disasters.

This system is not only a valuable tool for enhancing safety but also a great learning experience in microcontroller-based automation and embedded systems. It highlights the importance of accessible safety solutions in everyday life.